



# Alternating Current

Class 12 · Physics · Quick Revision · [chaptersnotes.in](https://chaptersnotes.in)

NEET: 2-3 Qs (~8-12 marks)

Boards: 6-8 marks



Scan: practise free

Current that reverses every half cycle: rms values, how R/L/C oppose and phase-shift it, how they combine in a series LCR circuit, resonance, real power, and the transformer.

## 1. AC, Peak & RMS Values

A sine source averages to zero over a cycle, so we rate it by its rms (heating-equivalent) value.

$$i = i_0 \sin(\omega t), \omega = 2\pi f$$

$i_0$  = peak,  $\omega$  = angular freq

$$I_{\text{rms}} = I_0/\sqrt{2} \approx 0.707 I_0$$

same  $I^2R$  heating as this DC

$$V_{\text{rms}} = V_0/\sqrt{2}$$

mains 220 V  $\rightarrow$   $V_0 \approx 311$  V

$$I_{\text{avg(half cycle)}} = 2I_0/\pi \approx 0.637 I_0$$

mean over half a cycle

**MUST KNOW** Full-cycle average of AC is ZERO; that is why rms (not mean) is used.

**MUST KNOW** AC ammeters/voltmeters already read rms - don't divide by  $\sqrt{2}$  again.

- A stated value (e.g. '5 A') is rms unless 'peak' or 'maximum' is specified.

## 2. AC Through R, L and C Separately

Each element has its own opposition (in ohms) and phase relation between V and I.

**Resistor: V, I in phase, opposition = R**

$\phi = 0$

$$X_L = \omega L = 2\pi fL$$

I lags V by  $90^\circ$ ; rises with f

$$X_C = 1/(\omega C) = 1/(2\pi fC)$$

I leads V by  $90^\circ$ ; falls with f

**MUST KNOW** Mnemonic CIVIL: in C, I leads V; in L, V leads I.

**MUST KNOW** At DC ( $f=0$ ):  $X_L = 0$  (coil = wire);  $X_C \rightarrow \infty$  (capacitor blocks DC).

- Pure L and pure C dissipate ZERO average power - reactance is not resistance.

## 3. Series LCR Circuit & Impedance

Same current, but  $V_R$ ,  $V_L$ ,  $V_C$  differ in phase, so add them as phasors - never arithmetically.

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

impedance, in ohms

$$V_{\text{rms}} = I_{\text{rms}} Z$$

AC Ohm's law

$$\tan\phi = (X_L - X_C)/R$$

phase angle V w.r.t I

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$V_L$ ,  $V_C$  are  $180^\circ$  apart  $\rightarrow$  subtract

**MUST KNOW**  $X_L > X_C \rightarrow$  inductive (V leads I);  $X_C > X_L \rightarrow$  capacitive (I leads V);  $X_L = X_C \rightarrow$  resistive.

**MUST KNOW**  $V_L$  or  $V_C$  can exceed the source voltage - perfectly normal, they largely cancel.

- Never write  $Z = R + (X_L - X_C)$ ; the terms add in quadrature (Pythagoras).

## 4. Resonance & Quality Factor

At one frequency  $X_L = X_C$  cancel; impedance is minimum and current maximum (acceptor circuit).

$$\omega_0 = 1/\sqrt{LC}, f_0 = 1/(2\pi\sqrt{LC})$$

depends only on L, C - not R

**At resonance:  $Z = R$  (min),  $I = V/R$  (max)**

$\cos\phi = 1$ , purely resistive

$$Q = (1/R)\sqrt{L/C} = \omega_0 L/R = 1/(\omega_0 CR)$$

sharpness of resonance

$$Q = f_0/\Delta f$$

$\Delta f$  = bandwidth

**MUST KNOW** Smaller R  $\rightarrow$  larger Q  $\rightarrow$  sharper, narrower peak  $\rightarrow$  better selectivity (radio tuning).

**MUST KNOW** R does NOT shift  $f_0$ ; it only sets the sharpness and the peak current.

- At resonance  $Z = R$  (a minimum), NOT zero - current stays finite at  $V/R$ .

## 5. Power & Power Factor (Wattless Current)

Real power depends on the phase: only the resistor consumes energy.

$$P = V_{\text{rms}} I_{\text{rms}} \cos\phi$$

true power (watts)

$$\cos\phi = R/Z$$

power factor

$$\text{Apparent power} = V_{\text{rms}} I_{\text{rms}}$$

volt-amperes (VA)

$$P = I_{\text{rms}}^2 R$$

reliable cross-check

**MUST KNOW** Pure L or C:  $\phi = 90^\circ$ ,  $\cos\phi = 0 \rightarrow$  wattless current (flows but consumes nothing).

**MUST KNOW** At resonance  $\cos\phi = 1$ , so power is maximum - not zero.

- Dropping  $\cos\phi$  gives apparent (not true) power - the classic blunder.

## 6. Transformer & LC Oscillations

Mutual induction reshapes AC voltage; an LC loop swaps energy between fields like an SHM.

$$V_s/V_p = N_s/N_p = I_p/I_s$$

ideal transformer

$$V_p I_p = V_s I_s$$

ideal: power conserved ( $\eta = 100\%$ )

$$\text{LC: } f = 1/(2\pi\sqrt{LC}), q = q_0 \cos(\omega_0 t)$$

$\omega_0 = 1/\sqrt{LC}$

**MUST KNOW** Works ONLY on AC - steady DC gives constant flux, so no induced emf.

**MUST KNOW** Step-up: voltage up, current down (and vice versa) - power can't be created.

- Iron loss cut by laminated core (eddy) + soft iron (hysteresis); copper loss =  $I^2 R$ .

## R vs L vs C in AC

| Element | Opposition         | Phase (I vs V)     | Power       |
|---------|--------------------|--------------------|-------------|
| R       | R                  | in phase           | $P = I^2 R$ |
| L       | $X_L = \omega L$   | I lags $90^\circ$  | zero        |
| C       | $X_C = 1/\omega C$ | I leads $90^\circ$ | zero        |

## Series LCR Behaviour

| Condition   | Nature                | Phase                       |
|-------------|-----------------------|-----------------------------|
| $X_L > X_C$ | Inductive             | V leads I                   |
| $X_C > X_L$ | Capacitive            | I leads V                   |
| $X_L = X_C$ | Resonance ( $Z = R$ ) | $\phi = 0$ , $\cos\phi = 1$ |

**Mnemonic - In C, I leads V; in L, V leads I - the phase relations for capacitor and inductor.**

CIVIL

## Common traps

- Full-cycle average of AC is zero;  $2I_0/\pi$  is the HALF-cycle mean. Don't swap them.
- AC meters read rms already - never divide a meter reading by  $\sqrt{2}$  again.
- Add  $V_R$ ,  $V_L$ ,  $V_C$  as phasors using  $(V_L - V_C)$ ; arithmetic sum is wrong.  $V_L/V_C$  may exceed the source.
- Power factor  $\cos\phi$  must be kept:  $P = V_{\text{rms}} I_{\text{rms}} \cos\phi$  is true power; without  $\cos\phi$  it is only apparent power. At resonance  $\cos\phi = 1$ , not 0.

## Most asked in NEET »

Peak  $\leftrightarrow$  rms ( $i_0/\sqrt{2}$ )

$X_L$ ,  $X_C$  and current in single elements

Impedance & power factor of series LCR

$V = \sqrt{(V_R)^2 + (V_L - V_C)^2}$

Resonant  $\omega_0$  /  $f_0$  & Q-factor

Transformer turns ratio & LC frequency

## Practise this chapter free

10+ real NEET PYQs with worked solutions, flashcards & a gamified app — all free at [chapternotes.in](https://www.chapternotes.in)

