



Current Electricity

Class 12 · Physics · Quick Revision · [chapternotes.in](https://www.chapternotes.in)

NEET: 2-3 Qs (~8-12 marks)

Boards: 7-9 marks



Scan: practise free

Charge in motion: how current flows, what resists it, how cells drive it, and the rules (Ohm, Kirchhoff) that solve any circuit.

1. Current, Drift & Ohm's Law

Current = rate of charge flow; drift velocity links it to electrons.

$$I = q / t$$

SI: ampere (A) - scalar

$$I = n A e v_d$$

microscopic current

$$v_d = (e E / m) \tau$$

τ = relaxation time

$$V = I R$$

Ohm's law

$$J = I / A = \sigma E$$

current density

- Conventional current is opposite to electron flow.

MUST KNOW Drift velocity is tiny (~mm/s) yet the bulb lights instantly - the field sets up at ~c.

- Mobility $\mu = v_d / E = e \tau / m$.

2. Resistance, Resistivity & Temperature

Resistance depends on material (ρ), geometry, and temperature.

$$R = \rho L / A$$

geometry

$$\rho = m / (n e^2 \tau)$$

microscopic resistivity

$$R_T = R_0 (1 + \alpha \Delta T)$$

α = temp. coeff.

MUST KNOW Resistivity ρ is a material property; resistance R is not (depends on L , A).

MUST KNOW Metals: ρ rises with temperature ($\alpha > 0$).
Semiconductors/insulators: ρ falls ($\alpha < 0$).

MUST KNOW On stretching a wire n times, R becomes n^2 times (volume constant).

3. Series & Parallel Combinations

Add resistances in series; add reciprocals in parallel.

$$\text{Series: } R = R_1 + R_2 + \dots$$

same current

$$\text{Parallel: } 1/R = 1/R_1 + 1/R_2 + \dots$$

same voltage

- Series: current same, voltage divides. Parallel: voltage same, current divides.

MUST KNOW Parallel R is always less than the smallest resistor.

4. EMF, Internal Resistance & Cells

A real cell has emf ϵ and internal resistance r .

$$\epsilon = I (R + r)$$

single cell

$$V = \epsilon - I r$$

terminal voltage (discharge)

$$\text{Series: } \epsilon = \sum \epsilon_i, r = \sum r_i$$

n cells

$$\text{Parallel (identical): } \epsilon_{eq} = \epsilon, r_{eq} = r/n$$

MUST KNOW Terminal $V < \epsilon$ while discharging; $V > \epsilon$ while charging; $V = \epsilon$ in open circuit.

MUST KNOW Max power transfer to load when $R = r$ ($P_{max} = \epsilon^2 / 4r$).

5. Kirchhoff, Wheatstone & Potentiometer

KCL + KVL solve any circuit; bridge & potentiometer are the classic instruments.

$$\text{KCL: } \sum I = 0 \text{ (junction)}$$

charge conservation

$$\text{KVL: } \sum V = 0 \text{ (loop)}$$

energy conservation

$$\text{Wheatstone balance: } P/Q = R/S$$

no galvanometer current

$$\text{Potentiometer: } \epsilon \propto l$$

balancing length

MUST KNOW At Wheatstone balance, no current flows through the galvanometer - bridge is independent of the cell.

MUST KNOW Potentiometer draws NO current at balance, so it measures true emf (unlike a voltmeter).

- Meter bridge = Wheatstone on a 1 m wire; balance: $R/S = l/(100 - l)$.

6. Electrical Power & Heating

Power dissipated and heat produced in a resistor.

$$P = V I = I^2 R = V^2 / R$$

pick by what's constant

$$H = I^2 R t$$

Joule heating

$$1 \text{ unit} = 1 \text{ kWh} = 3.6 \times 10^6 \text{ J}$$

commercial energy

MUST KNOW Series bulbs: same I , so higher- R bulb glows brighter.
Parallel: same V , so lower- R bulb glows brighter.

- A bulb rated (P , V) has $R = V^2 / P$ - use rated values to find R .

Series vs Parallel

	Series	Parallel
Current	Same in all	Divides
Voltage	Divides	Same across all
Net R	Sum (largest)	< smallest
Use	Current control	Constant voltage

**Mnemonic - Resistor colour code 0-9: Black Brown Red Orange
Yellow Green Blue Violet Grey White**

B B ROY of Great Britain had a Very Good Wife

Terminal Voltage of a Cell

State	Relation
Discharging	$V = \epsilon - Ir$ ($V < \epsilon$)
Charging	$V = \epsilon + Ir$ ($V > \epsilon$)
Open circuit	$V = \epsilon$ ($I = 0$)

Common traps

- Drift velocity is small, but current and the field travel near light-speed - don't confuse the two.
- Ammeter = LOW resistance, in SERIES. Voltmeter = HIGH resistance, in PARALLEL. Swapping them is the classic blunder.
- Resistivity ρ is intrinsic (no L or A). Only resistance R changes with shape.
- Internal resistance r is in series with the load - forgetting it gives wrong I.

Most asked in NEET »

Drift velocity / mobility

Stretched-wire $R \rightarrow n^2$

Wheatstone & meter bridge balance

Potentiometer (emf vs voltmeter)

Combination of cells

Bulb brightness in series/parallel

Practise this chapter free

10+ real NEET PYQs with worked solutions, flashcards & a gamified app — all free at [chapternotes.in](https://www.chapternotes.in)

